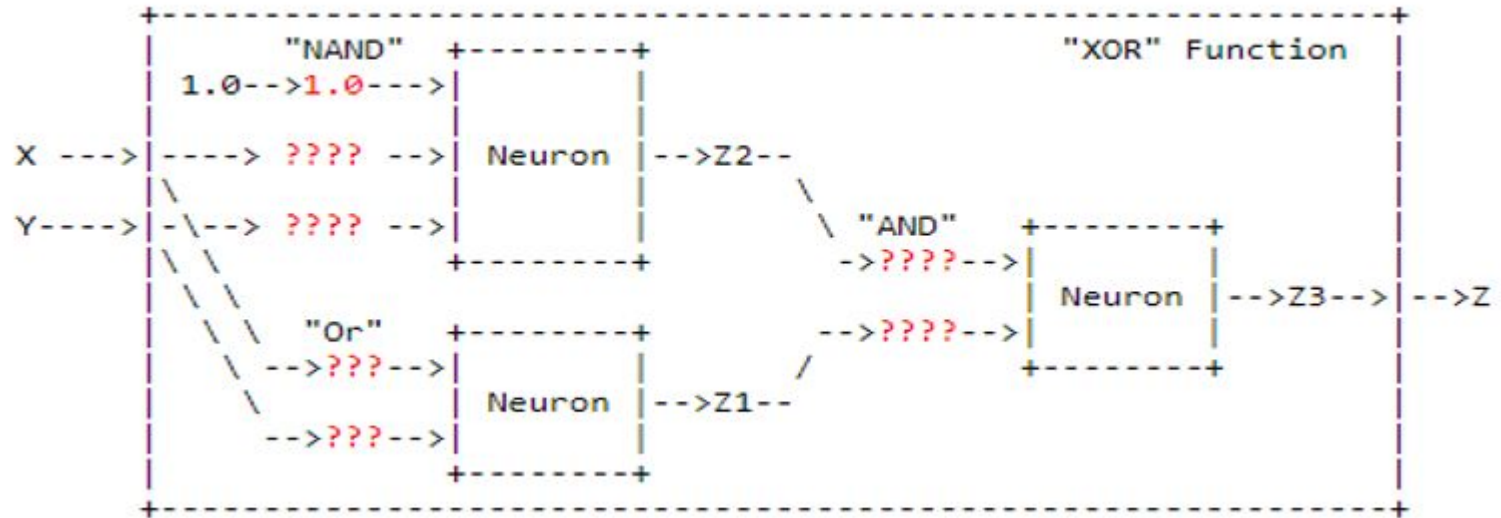



# ML Project: Design XOR Gate



# ML Project: Design XOR Gate
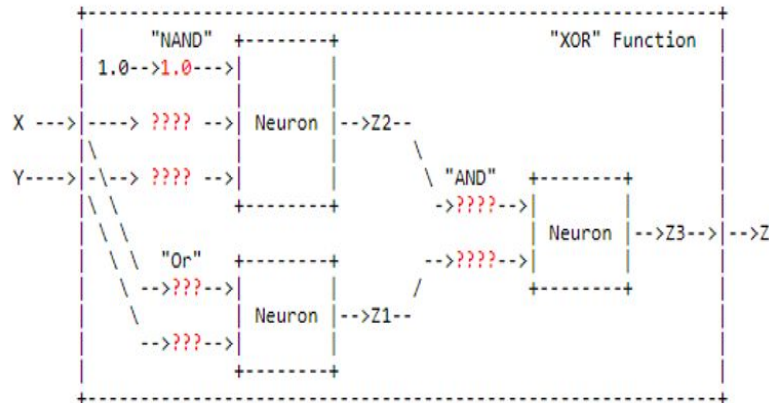
## Step 1: How to design [XOR Gate](#)

- Construct the truth table for XOR
- Obtain the network equation



- Construct the truth table for XOR

- The truth-table for the "XOR" function.

OR				NAND				XOR		
X	Y	Z1		X	Y	Z2		X	Y	Z3
0	0	0		0	0	1		0	0	0
0	1	1	AND	0	1	1	=	0	1	1
1	0	1		1	0	1		1	0	1
1	1	1		1	1	0		1	1	0

- Obtain the network equation

The neural network equation can be created by combining neural equations.

$$Z1 := X \text{ "Or" } Y$$


$$Z2 := X \text{ "NAND" } Y$$

$$Z := Z3 := Z1 \text{ "AND" } Z2$$


$$Z := (X \text{ "Or" } Y) \text{ "AND" } (X \text{ "NAND" } Y)$$
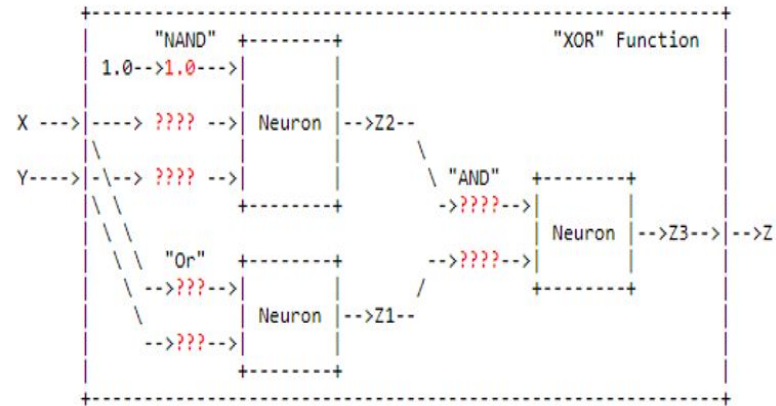
# ML Project: Design XOR Gate

Step 2: Calculate Z1, Z2, and Z3 transfer functions



a.  $Z1 := X \text{ "NAND" } Y$

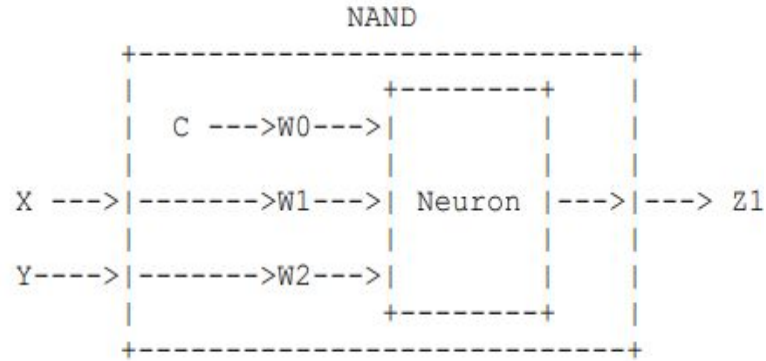

$$Z1 := (W0 * C + W1 * X + W2 * Y \geq T)$$


Train NAND gate to get **w0, w1, w2** ?

$$Z := Z1 = (W0 * C + W1 * X + W2 * Y \geq T)$$

where  $T := 1.0$ .
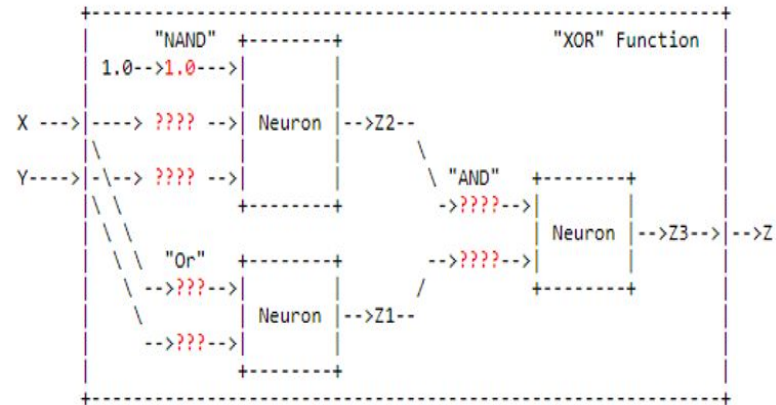
# ML Project: Design XOR Gate

Step 2: Calculate Z1, Z2, and Z3 transfer functions




a.  $Z1 := X \text{ "NAND" } Y$


<p>Desired "NAND" Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </table>	C	X	Y	Z	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	<p>Loop 1 W0=0.0 W1=W2=0.5 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </table>	C	X	Y	Z	1	0	0	0	1	0	1	0	1	1	0	0	1	1	1	0	<p>Loop 2 W0=0 W1=W2=1 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </table>	C	X	Y	Z	1	0	0	0	1	0	1	1	1	1	0	1	1	1	1	1	<p>Loop 3 W0=0.5 W1=W2=1 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </table>	C	X	Y	Z	1	0	0	0	1	0	1	1	1	1	0	1	1	1	1	1
C	X	Y	Z																																																																																
1	0	0	1																																																																																
1	0	1	1																																																																																
1	1	0	1																																																																																
1	1	1	0																																																																																
C	X	Y	Z																																																																																
1	0	0	0																																																																																
1	0	1	0																																																																																
1	1	0	0																																																																																
1	1	1	0																																																																																
C	X	Y	Z																																																																																
1	0	0	0																																																																																
1	0	1	1																																																																																
1	1	0	1																																																																																
1	1	1	1																																																																																
C	X	Y	Z																																																																																
1	0	0	0																																																																																
1	0	1	1																																																																																
1	1	0	1																																																																																
1	1	1	1																																																																																
<p>Loop 4 W0= 1 W1=W2=1 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </table>	C	X	Y	Z	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	1	<p>Loop 5 W0= 1 W1=W2=0.5 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </table>	C	X	Y	Z	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	1	<p>Loop 6 W0= 1 W1=W2=0 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </table>	C	X	Y	Z	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	1	<p>Loop 7 W0= 1 W1=W2=-0.5 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </table>	C	X	Y	Z	1	0	0	1	1	0	1	0	1	1	0	0	1	1	1	0
C	X	Y	Z																																																																																
1	0	0	1																																																																																
1	0	1	1																																																																																
1	1	0	1																																																																																
1	1	1	1																																																																																
C	X	Y	Z																																																																																
1	0	0	1																																																																																
1	0	1	1																																																																																
1	1	0	1																																																																																
1	1	1	1																																																																																
C	X	Y	Z																																																																																
1	0	0	1																																																																																
1	0	1	1																																																																																
1	1	0	1																																																																																
1	1	1	1																																																																																
C	X	Y	Z																																																																																
1	0	0	1																																																																																
1	0	1	0																																																																																
1	1	0	0																																																																																
1	1	1	0																																																																																
<p>Loop 7 W0= 1.5 W1=W2=-0.5 Function</p> <table> <tr><th>C</th><th>X</th><th>Y</th><th>Z</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </table>	C	X	Y	Z	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	<p>Therefor :</p> <p><b>W0= 1.5, W1=W2=-0.5</b></p> <p><b><math>Z1 := ( 1.5 * 1.0 + -0.5 * X + -0.5 * Y \geq 1.0 )</math></b></p>																																																														
C	X	Y	Z																																																																																
1	0	0	1																																																																																
1	0	1	1																																																																																
1	1	0	1																																																																																
1	1	1	0																																																																																
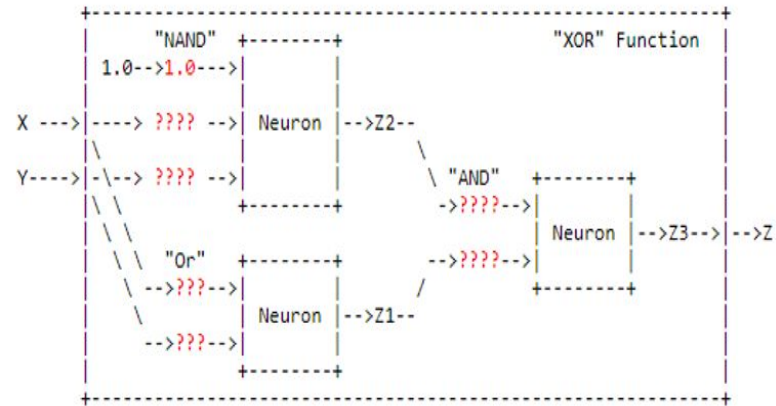
# ML Project: Design XOR Gate

Step 2: Calculate Z1, Z2, and Z3 transfer functions



b.  $Z2 := X \text{ "or" } Y$

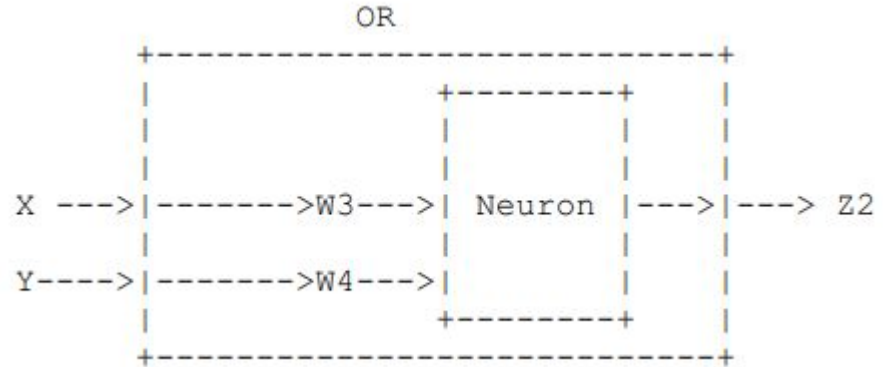

$$Z2 := (W3 * X + W4 * Y \geq T)$$


Train NAND gate to get  $w3, w4$  ?

$$Z2 := (W3 * X + W4 * Y \geq T)$$

where  $T = 1.0$ .
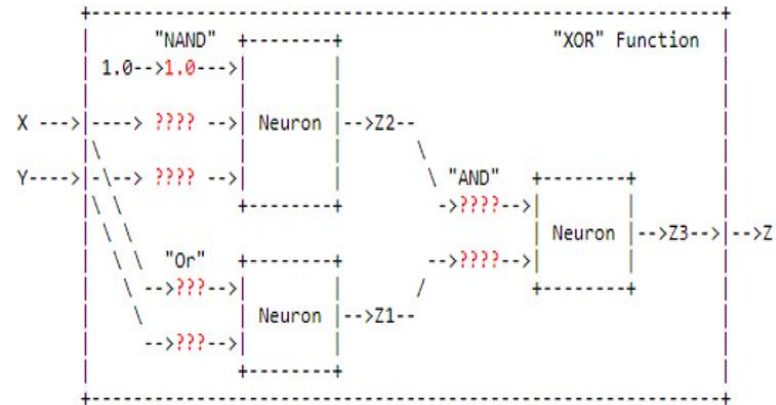
# ML Project: Design XOR Gate

Step 2: Calculate Z1, Z2, and Z3 transfer functions



b.  $Z2 := X \text{ "or" } Y$

Desired "OR" Function	Loop 1 $W3=W4=0.5$ Function	Loop 2 $W3=W4=1$ Function
X Y   Z	X Y   Z	X Y   Z
0 0   0	0 0   0	0 0   0
0 1   1	0 1   0	0 1   1
1 0   1	1 0   0	1 0   1
1 1   1	1 1   1	1 1   1


Therefor:

$W3=W4=1$


$Z2 := (1 * X + 1 * Y >= 1.0)$
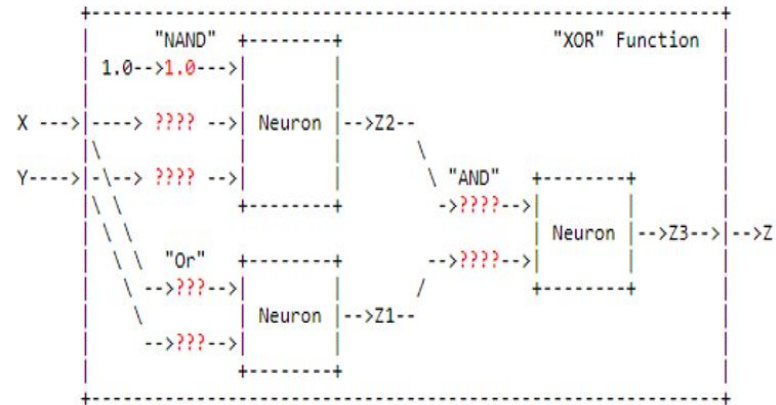
# ML Project: Design XOR Gate

Step 2: Calculate Z1, Z2, and Z3 transfer functions



c.  $Z := Z3 := Z1 \text{ "AND" } Z2$

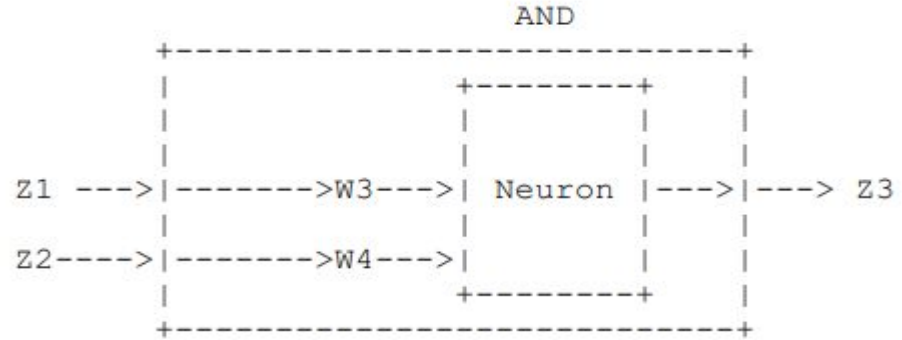

$$Z3 := (W5 * Z1 + W6 * Z2 \geq T)$$

Train the AND gate to get w5, W6


let  $Z1 := X$ , and  $Z2 := Y$

$$Z3 := (W5 * X + W6 * Y \geq T)$$

where  $T := 1.0$ .
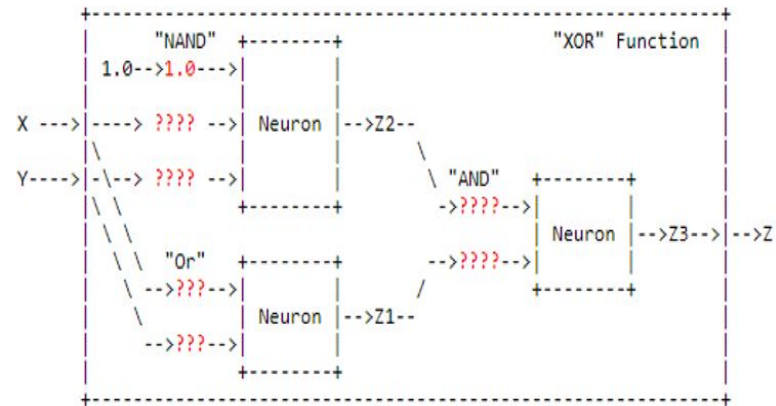
# ML Project: Design XOR Gate

Step 2: Calculate Z1, Z2, and Z3 transfer functions



c.  $Z := Z3 := Z1 \text{ "AND" } Z2$

Desired "AND" Function	Loop 1 $W4=W5=0.5$ Function
X Y   Z	X Y   Z
0 0   0	0 0   0
0 1   0	0 1   0
1 0   0	1 0   0
1 1   1	1 1   1

**Therefor:**


$W5=W6= 0.5$

$Z3: = (0.5* X + 0.5* Y \geq 1.0 ) = (0.5* Z1 + 0.5* Z2 \geq 1.0 )$


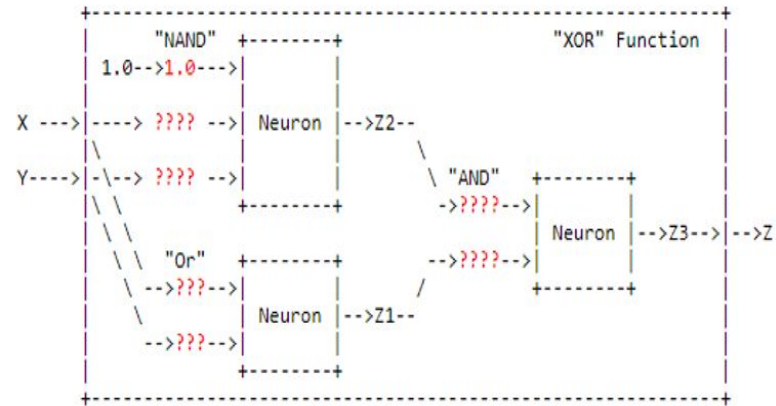
# ML Project: Design XOR Gate

Step 2: Calculate Z1, Z2, and Z3 transfer functions



D. Complete XOR neural network circuit diagram

$$W0 = 1.5, W1 = W2 = -0.5$$


$$Z1 = (1.5 * 1.0 + -0.5 * X + -0.5 * Y \geq 1.0)$$

$$W3 = W4 = 1$$

$$Z2 = (1 * X + 1 * Y \geq 1.0)$$


$$W5 = W6 = 0.5$$
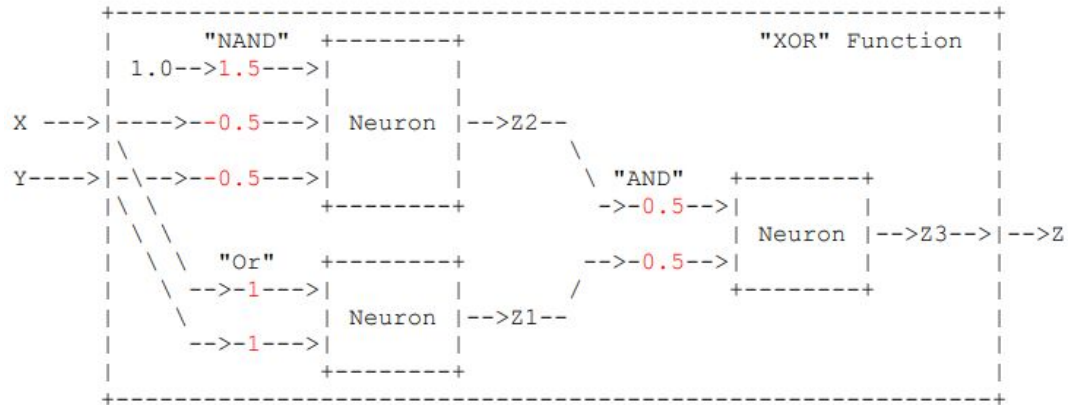
$$Z3 = (0.5 * X + 0.5 * Y \geq 1.0) = (0.5 * Z1 + 0.5 * Z2 \geq 1.0)$$



# ML Project: Design XOR Gate

## Step 3: Prove results

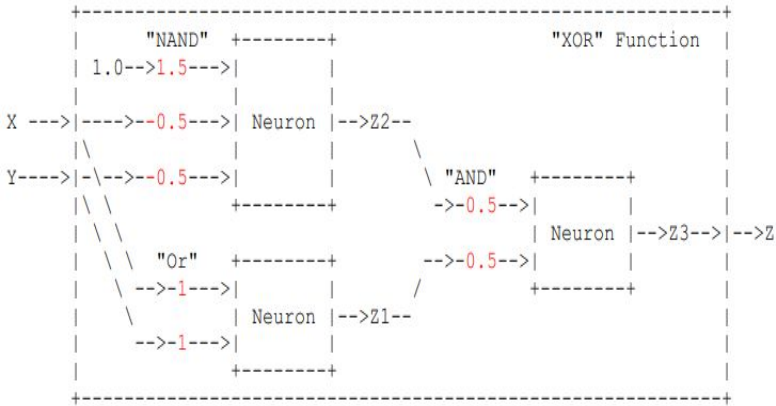

### Prove result:


Test cases:

- X=1, Y=1
- X=1, Y=0
- X=0, Y=1
- X=0, Y=0

Test 1: X=1, Y=1	Desired Result																								
<div>Z1: = ( 1.5 * 1.0 + -0.5 * X + -0.5 * Y &gt;= 1.0 ) = 1.5-0.5-0.5 := 0</div> <div>Z2: = (1* X + 1* Y &gt;= 1.0 ) = 1 + 1 := 1</div> <div>Z3: = (0.5* Z1 + 0.5* Z2 &gt;= 1.0 ) = 0.5*0 + 0.5*1 := 0</div>	<div>XOR</div> <div>-----</div> <table><tr><td>X</td><td>Y</td><td> </td><td>Z</td></tr><tr><td colspan="4">-----</td></tr><tr><td>0</td><td>0</td><td> </td><td>0</td></tr><tr><td>0</td><td>1</td><td> </td><td>1</td></tr><tr><td>1</td><td>0</td><td> </td><td>1</td></tr><tr><td>1</td><td>1</td><td> </td><td>0</td></tr></table>	X	Y		Z	-----				0	0		0	0	1		1	1	0		1	1	1		0
X	Y		Z																						
-----																									
0	0		0																						
0	1		1																						
1	0		1																						
1	1		0																						
Test 2: X=1, Y=0	Desired Result																								
<div>Z1: = ( 1.5 * 1.0 + -0.5 * X + -0.5 * Y &gt;= 1.0 ) = 1.5-0.5*1-0.5*0 := 1</div> <div>Z2: = (1* X + 1* Y &gt;= 1.0 ) = 1*1 + 1*0 := 1</div> <div>Z3: = (0.5* Z1 + 0.5* Z2 &gt;= 1.0 ) = 0.5*1 + 0.5*1 := 1</div>	<div>XOR</div> <div>-----</div> <table><tr><td>X</td><td>Y</td><td> </td><td>Z</td></tr><tr><td colspan="4">-----</td></tr><tr><td>0</td><td>0</td><td> </td><td>0</td></tr><tr><td>0</td><td>1</td><td> </td><td>1</td></tr><tr><td>1</td><td>0</td><td> </td><td>1</td></tr><tr><td>1</td><td>1</td><td> </td><td>0</td></tr></table>	X	Y		Z	-----				0	0		0	0	1		1	1	0		1	1	1		0
X	Y		Z																						
-----																									
0	0		0																						
0	1		1																						
1	0		1																						
1	1		0																						

# ML Project: Design XOR Gate

## Step 3: Prove results

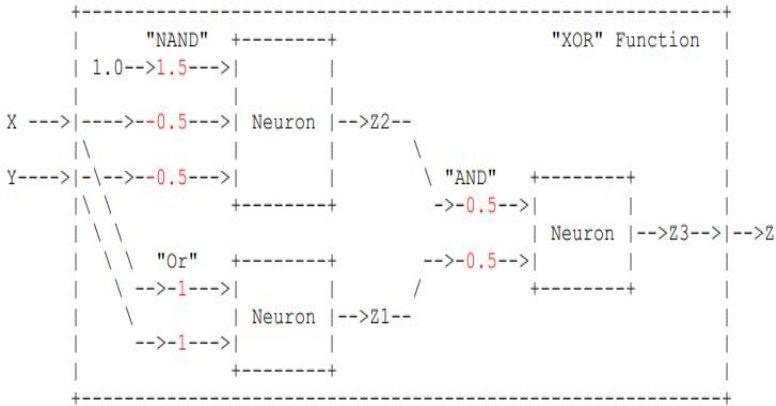

### Prove result:

Test cases:

- X=1, Y=1
- X=1, Y=0
- X=0, Y=1
- X=0, Y=0

Test 3: X=0, Y=1	Desired Result
$Z1: = ( 1.5 * 1.0 + -0.5 * X + -0.5 * Y \geq 1.0 )$ $= 1.5*1.0-0.5*0-0.5*1 := 1$ $Z2: = (1* X + 1* Y \geq 1.0 )$ $= 1*0 + 1*1 := 1$ $Z3: = (0.5* Z1 + 0.5* Z2 \geq 1.0 )$ $= 0.5*1 + 0.5*1 := 1$	XOR ----- X Y   Z ----- 0 0   0 0 1   1 1 0   1 1 1   0
Test 2: X=0, Y=0	Desired Result
$Z1: = ( 1.5 * 1.0 + -0.5 * X + -0.5 * Y \geq 1.0 )$ $= 1.5-0.5*0-0.5*0 := 1$ $Z2: = (1* X + 1* Y \geq 1.0 )$ $= 1*0 + 1*0 := 0$ $Z3: = (0.5* Z1 + 0.5* Z2 \geq 1.0 )$ $= 0.5*1 + 0.5*0 := 0$	XOR ----- X Y   Z ----- 0 0   0 0 1   1 1 0   1 1 1   0

# ML Project: Design XOR Gate

## Conclusion:

The test results obtained based on the final parameters agree with the desired values. Hence, for the given XOR gate, below are the final parameters values and the complete ANN circuit diagram.

$W_0 = 1.5$

$W_1 = W_2 = -0.5$

$W_3 = W_4 = 1$

$W_5 = W_6 = 0.5$

